

Electronics and Instrumentations

Operational Amplifiers (Op-Amps)

K. THAMILMARAN




Department of Nonlinear Dynamics
School of Physics, Bharathidasan University
Tiruchirapalli-620 024
maran.cnld@gamil.com

Operational Amplifiers (Op Amps)

- **Ideal Op Amp**
- Non-inverting Amplifier
- Unity-Gain Buffer
- Inverting Amplifier
- Differential Amplifier
- Current-to-Voltage Converter
- Non-ideal Op Amp

Ideal Op Amp

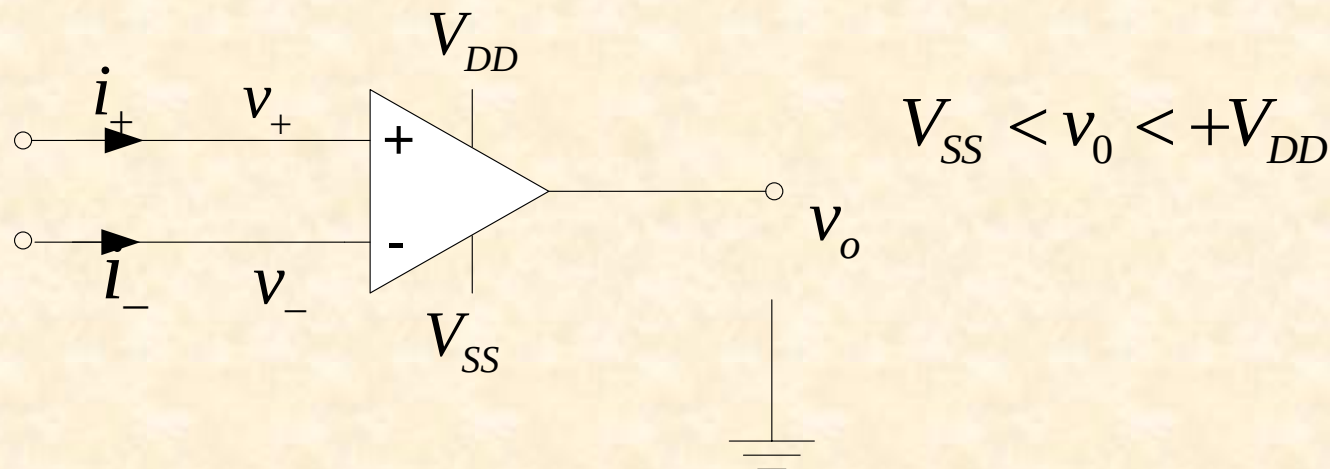


$$1) \quad v_o = A_v (v_+ - v_-)$$

The open-loop gain, A_v , is very large, approaching infinity.

$$2) \quad i_+ = i_- = 0$$

The current into the inputs are zero.

Ideal Op Amp with Negative Feedback

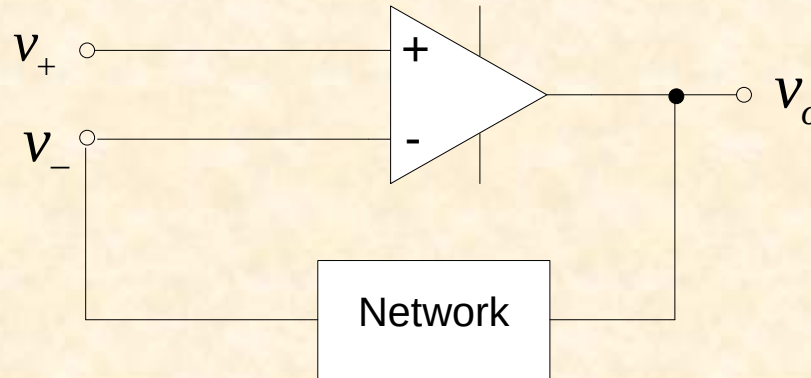


Golden Rules of Op Amps:

1. The output attempts to do whatever is necessary to make the voltage difference between the inputs zero.
2. The inputs draw no current.

Operational Amplifiers (Op Amps)

- Ideal Op Amp
- **Non-inverting Amplifier**
- Unity-Gain Buffer
- Inverting Amplifier
- Differential Amplifier
- Current-to-Voltage Converter
- Non-ideal Op Amp

Non-inverting Amplifier

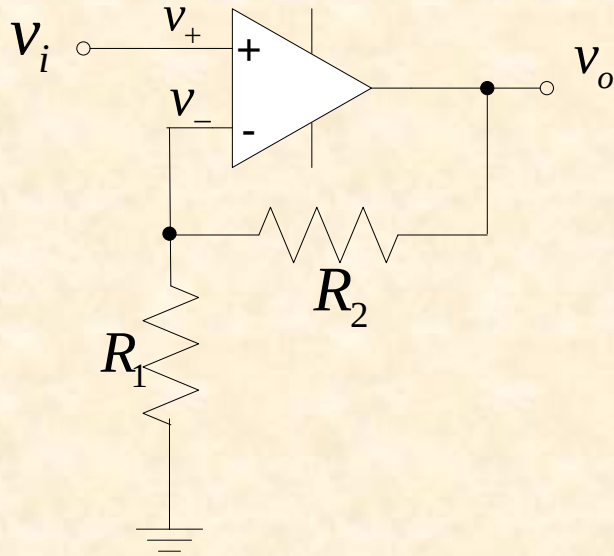

Closed-loop voltage gain

$$A_F = \frac{v_o}{v_i}$$


$$v_i = v_+ = v_- = \frac{R_1}{R_1 + R_2} v_o$$

$$A_F = \frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$

Operational Amplifiers (Op Amps)

- Ideal Op Amp
- Non-inverting Amplifier
- **Unity-Gain Buffer**
- Inverting Amplifier
- Differential Amplifier
- Current-to-Voltage Converter
- Non-ideal Op Amp

Unity-Gain Buffer

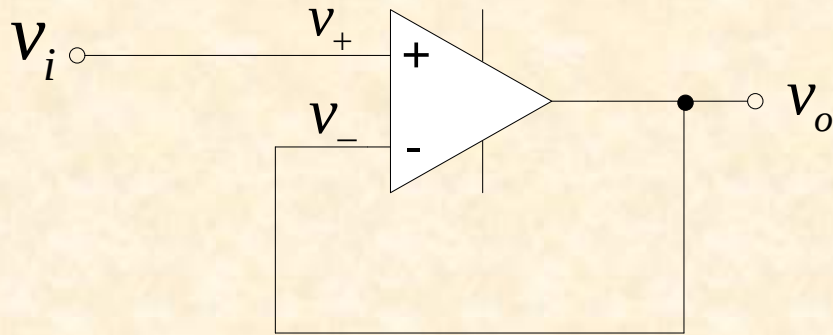

Closed-loop voltage gain

$$A_F = \frac{V_o}{V_i}$$

$$V_i = V_+ = V_- = V_o$$

$$A_F = \frac{V_o}{V_i} = 1$$


Used as a "line driver" that transforms a high input impedance (resistance) to a low output impedance. Can provide substantial current gain.

Operational Amplifiers (Op Amps)

- Ideal Op Amp
- Non-inverting Amplifier
- Unity-Gain Buffer
- **Inverting Amplifier**
- Differential Amplifier
- Current-to-Voltage Converter
- Non-ideal Op Amp

Inverting Amplifier

Current into op amp is zero

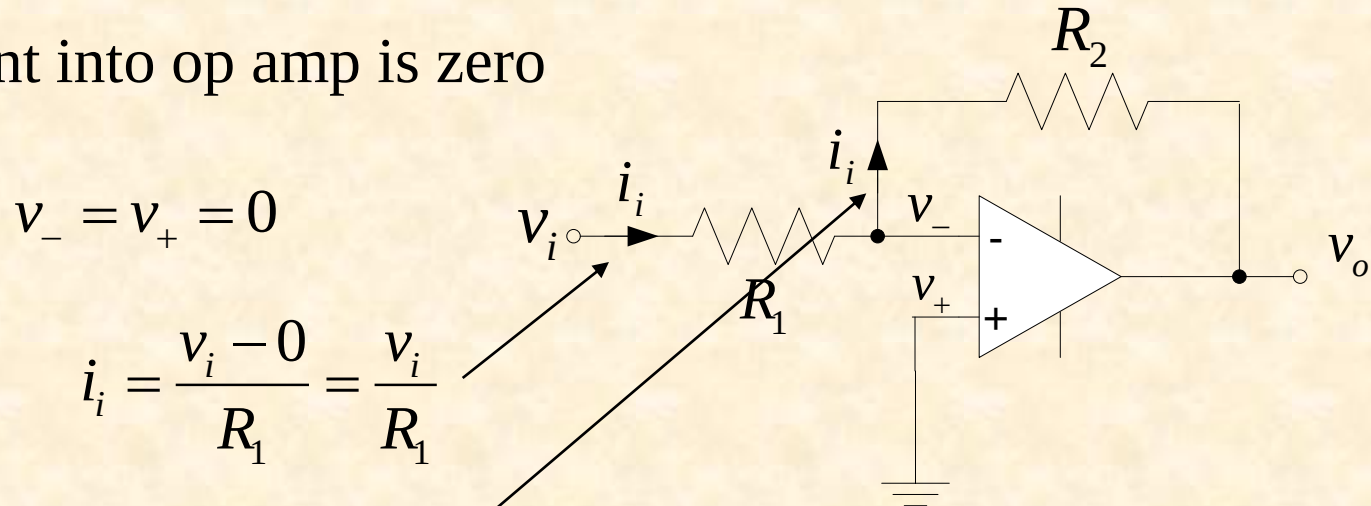

$$v_- = v_+ = 0$$

$$i_i = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1}$$

$$i_i = \frac{0 - v_o}{R_2} = \frac{-v_o}{R_2}$$

$$\frac{v_i}{R_1} = \frac{-v_o}{R_2}$$


$$A_F = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

Operational Amplifiers (Op Amps)

- Ideal Op Amp
- Non-inverting Amplifier
- Unity-Gain Buffer
- Inverting Amplifier
- **Differential Amplifier**
- Current-to-Voltage Converter
- Non-ideal Op Amp

Differential Amplifier

Current into op amp is zero

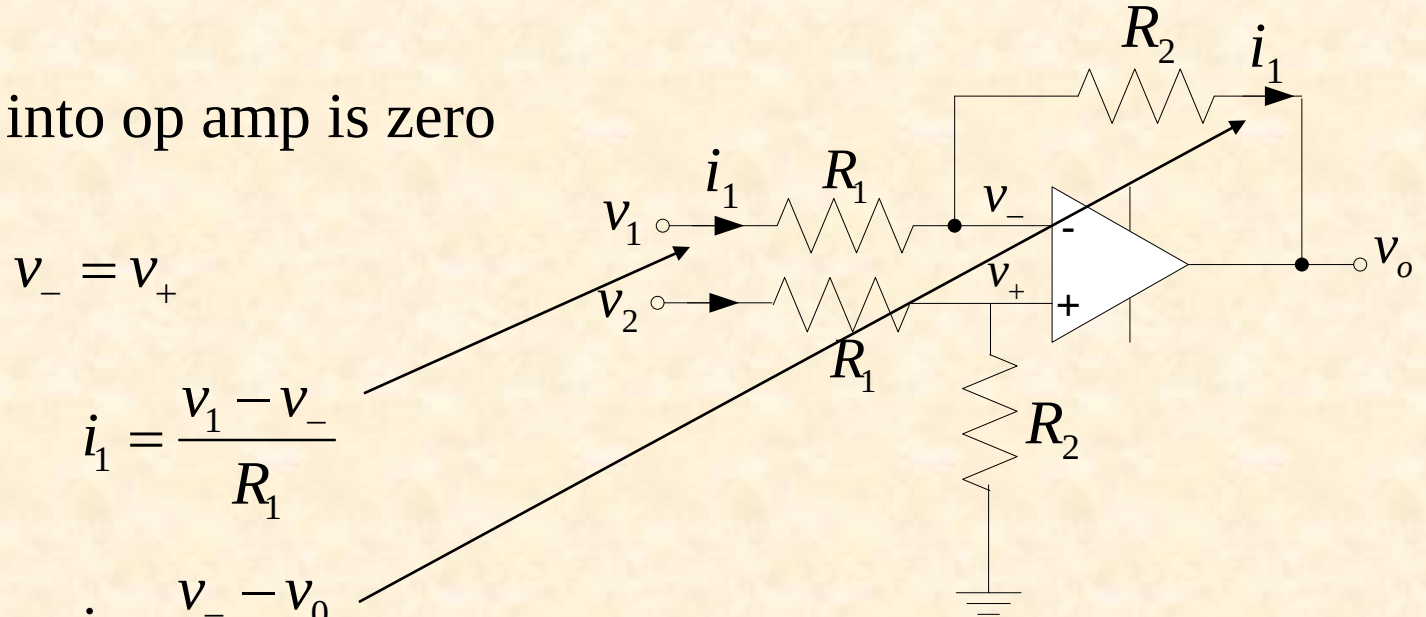

$$v_- = v_+$$

$$i_1 = \frac{v_1 - v_-}{R_1}$$

$$i_1 = \frac{v_- - v_o}{R_2}$$

$$\frac{v_1 - v_+}{R_1} = \frac{v_+ - v_o}{R_2}$$

$$v_+ = \frac{R_2}{R_1 + R_2} v_2$$

$$\frac{v_1 - \frac{R_2}{R_1 + R_2} v_2}{R_1} = \frac{\frac{R_2}{R_1 + R_2} v_2 - v_o}{R_2}$$


Differential Amplifier

$$\frac{v_1 - \frac{R_2}{R_1 + R_2} v_2}{R_1} = \frac{\frac{R_2}{R_1 + R_2} v_2 - v_0}{R_2}$$

$$v_0 = -\frac{R_2}{R_1} v_1 + \frac{R_2}{R_1 + R_2} v_2 + \frac{R_2^2}{R_1(R_1 + R_2)} v_2$$

$$v_0 = -\frac{R_2}{R_1} v_1 + \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_2}{R_1} \right) v_2$$


$$v_0 = \frac{R_2}{R_1} (v_2 - v_1)$$

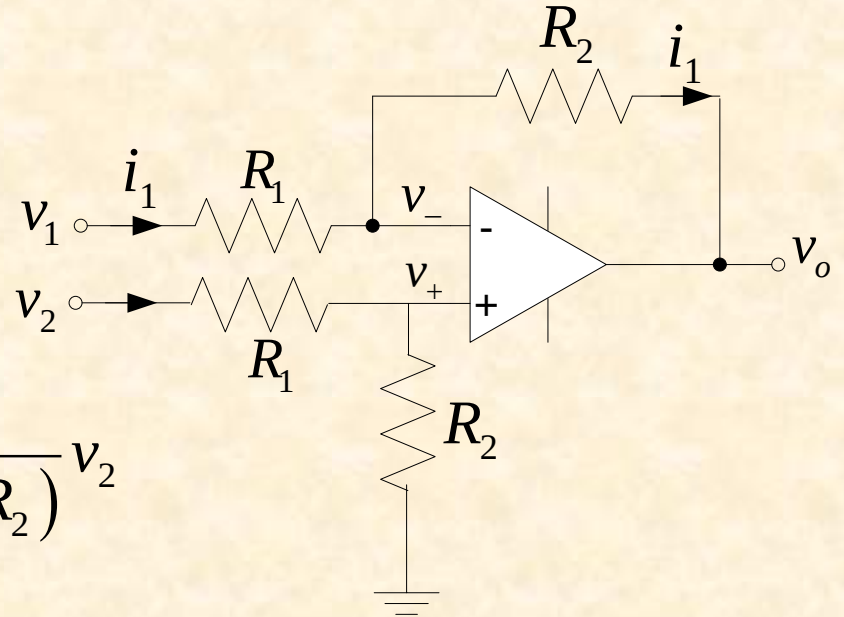

Operational Amplifiers (Op Amps)

- Ideal Op Amp
- Non-inverting Amplifier
- Unity-Gain Buffer
- Inverting Amplifier
- Differential Amplifier
- **Current-to-Voltage Converter**
- Non-ideal Op Amp

Current-to-Voltage Converter

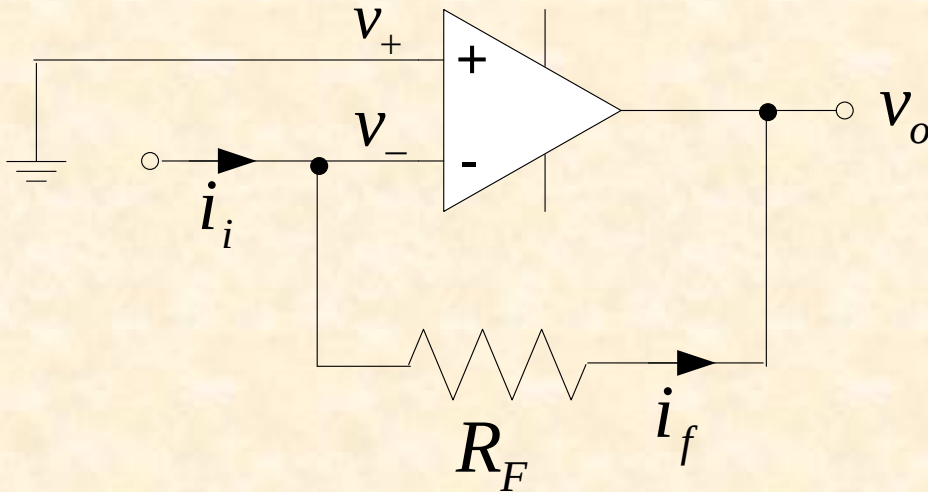

$$i_i = i_f$$

$$v_- = v_+ = 0$$


$$0 - v_o = i_f R_F$$

$$v_o = -i_i R_F$$

$$\text{Transresistance} = \Delta v_o / \Delta i_i = -R_F$$

Photodiode Circuit

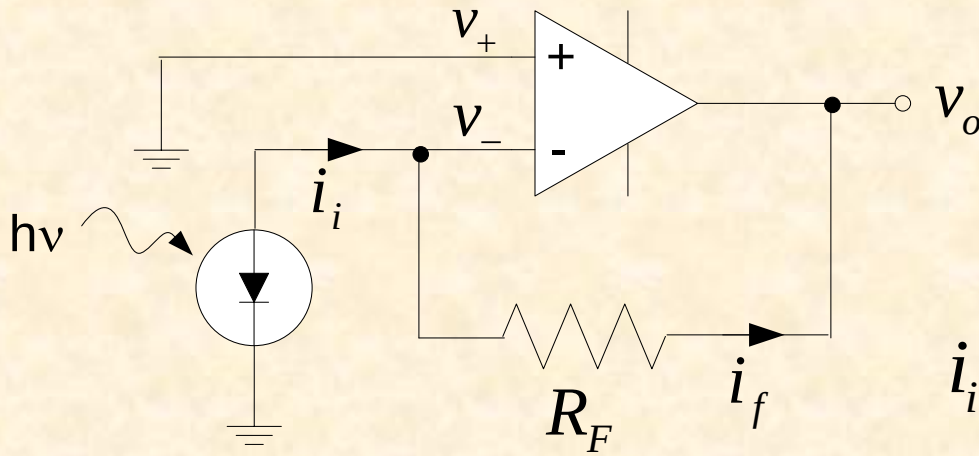$i_i = 25\mu\text{A}$ per milliwatt of incident radiation



At 50 mW

$$i_i = 50 \times 25 \times 10^{-6} = 1.25\text{mA}$$

Assume $R_F = 3.2\text{k}\Omega$

$$v_o = -i_i R_F = -1.25 \times 10^{-3} \times 3.2 \times 10^3 = -4\text{V}$$

Operational Amplifiers (Op Amps)

- Ideal Op Amp
- Non-inverting Amplifier
- Unity-Gain Buffer
- Inverting Amplifier
- Differential Amplifier
- Current-to-Voltage Converter
- **Non-ideal Op Amp**

Non-ideal Op Amp

- Output voltage is limited by supply voltage(s)
- Finite gain ($\sim 10^5$)
- Limited frequency response
- Finite input resistance (not infinite)
- Finite output resistance (not zero)
- Finite slew rate slew rate $= dv_0(t)/dt_{MAX}$
- Input bias currents
- Input bias current offset
- Input offset voltage
- Finite common mode rejection ratio (CMRR)